

4.0 PRE-LAB ASSIGNMENT (3 marks with 1.5 marks for each step):

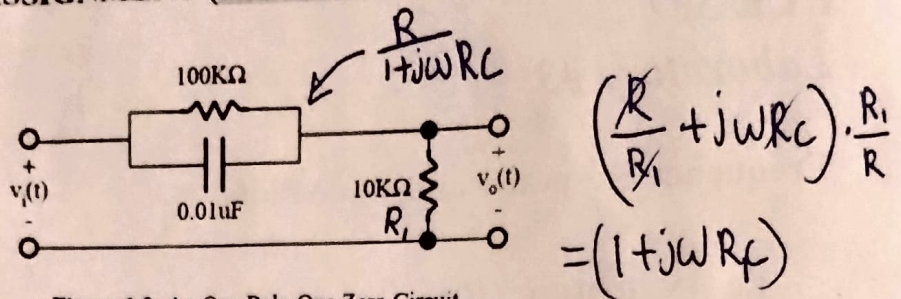


Figure 1.0: An One Pole-One Zero Circuit

(a) Step 1: Consider the network shown in Figure 1.0.

- i) Derive the transfer function $H(s) = V_o/V_i$, where V_o is the phasor representation of $v_o(t)$ and V_i is the phasor representation of $v_i(t)$.

Pre-Lab workspace (show your analysis here)

$$H(\omega) = \frac{V_o}{V_i} \Rightarrow V_o = \frac{R_i}{R_i + \frac{R}{1+j\omega RC}} V_i = \frac{R_i (1+j\omega RC)}{(R_i + \frac{R}{1+j\omega RC})(1+j\omega RC)}$$

$$\frac{R_i (1+j\omega RC)}{R_i (1+j\omega RC) + R} \Rightarrow \frac{1+j\omega RC}{1+j\omega RC + \frac{R}{R_i}} \quad \text{Since } \frac{R}{R_i} = 100 \Rightarrow \frac{1+j\omega RC}{\frac{R}{R_i} + j\omega RC} \times \frac{R_i}{R}$$

$$\frac{V_o}{V_i} = \frac{10k}{100k} \cdot \frac{1+j\omega \frac{1}{1000}}{1+j\omega \frac{1}{10000}} \cdot \frac{1}{RC}$$

$$\frac{V_o}{V_i} = 0.1 \frac{1+j\omega \frac{1}{1000}}{1+j\omega \frac{1}{10000}}$$

Annotations: The term $\frac{R_i}{R}$ is labeled "Constant". The term $\frac{1+j\omega RC}{1+j\omega R_f}$ is labeled "pole" and "zero".

$$\textcircled{1} \leftarrow \textcircled{0.1} \frac{1+j\omega}{1+j\frac{\omega}{10000}} \textcircled{2}$$

$$20 \log(0.1) = -20 \text{ dB}$$


② —

③ — ④ —

② ~~pass~~ final

② + ③

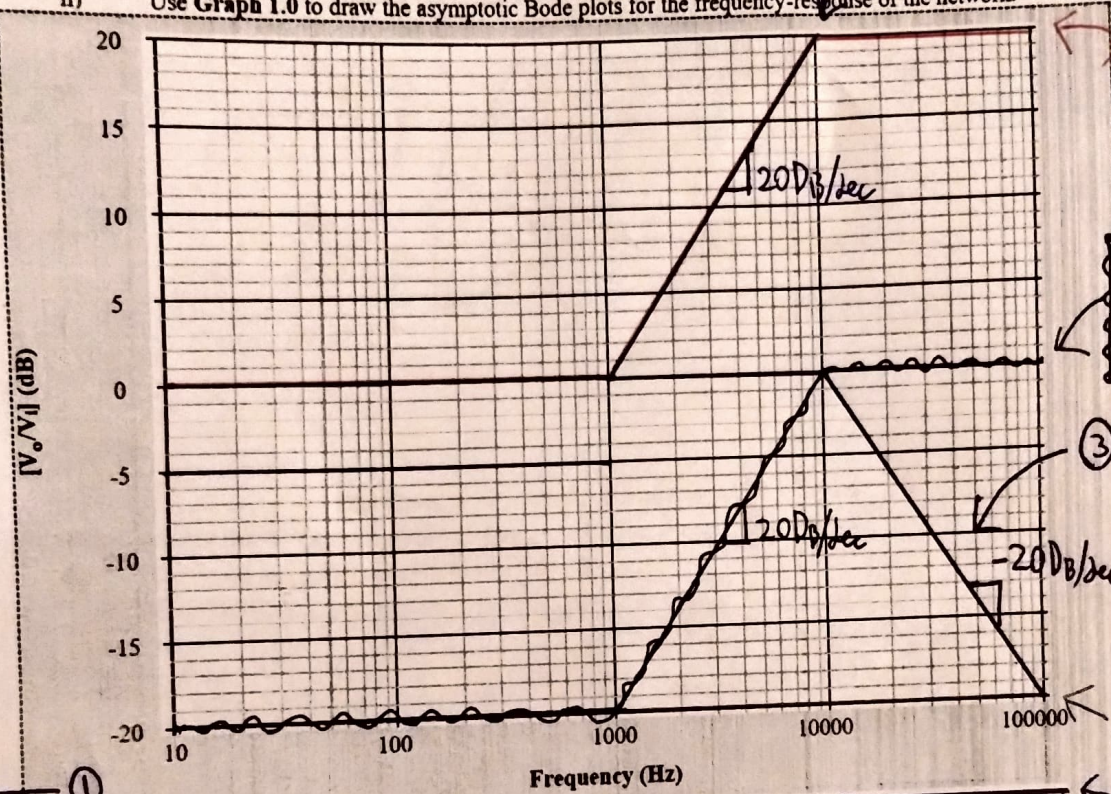ii) Use Graph 1.0 to draw the asymptotic Bode plots for the frequency-response of the network.



$$0.1 = 0^\circ$$


$$\angle \left(\frac{1+j\omega}{1+j\frac{\omega}{10000}} \right)$$

$$\frac{1}{1+j\frac{\omega}{10000}}$$

final — ③

$$\frac{1+j\omega}{1+j\frac{\omega}{10000}}$$

$$\frac{1}{1+j\frac{\omega}{10000}}$$

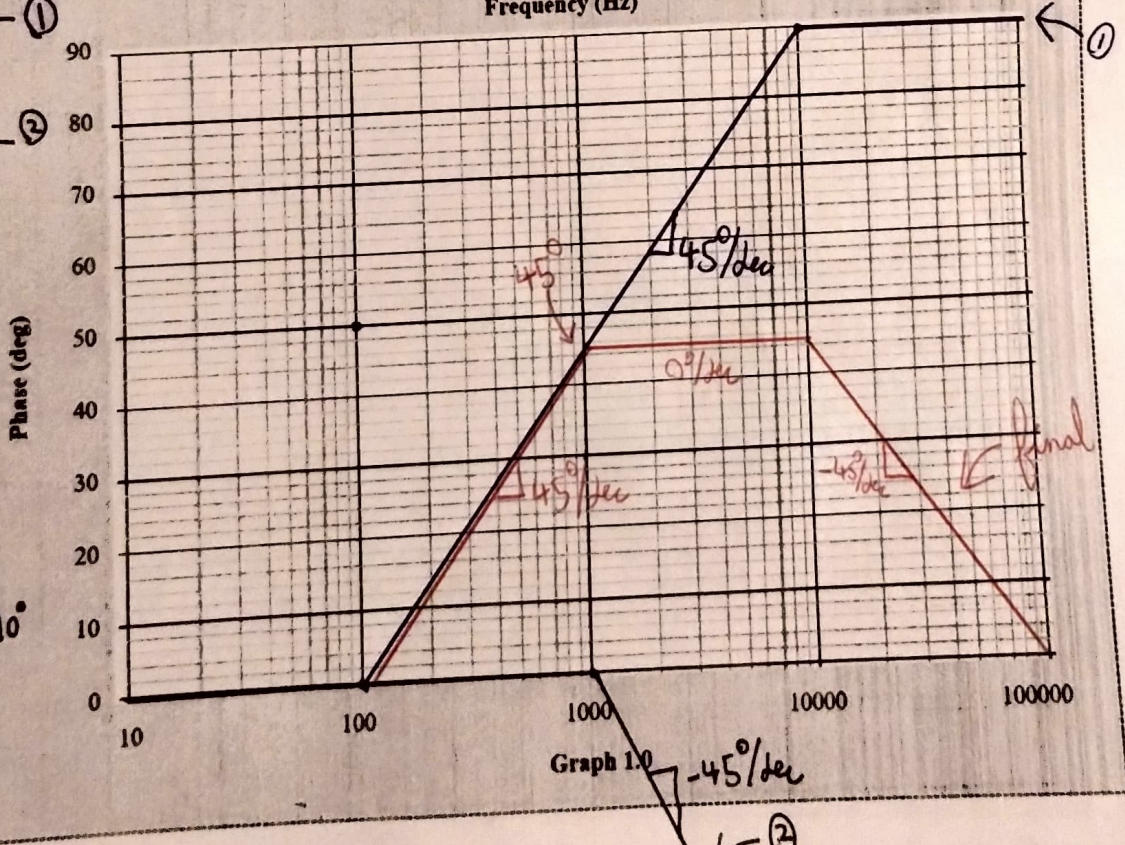


Graph 1.0

③

- iii) Use Multisim to plot the magnitude in dB and phase in degrees of the frequency-responses of the above circuits, for $10\text{Hz} \leq f \leq 100\text{kHz}$. (Note: Simulate->Instruments->Bode Plotter can be used in creating the plots).

Pre-Lab workspace (show your analysis here)

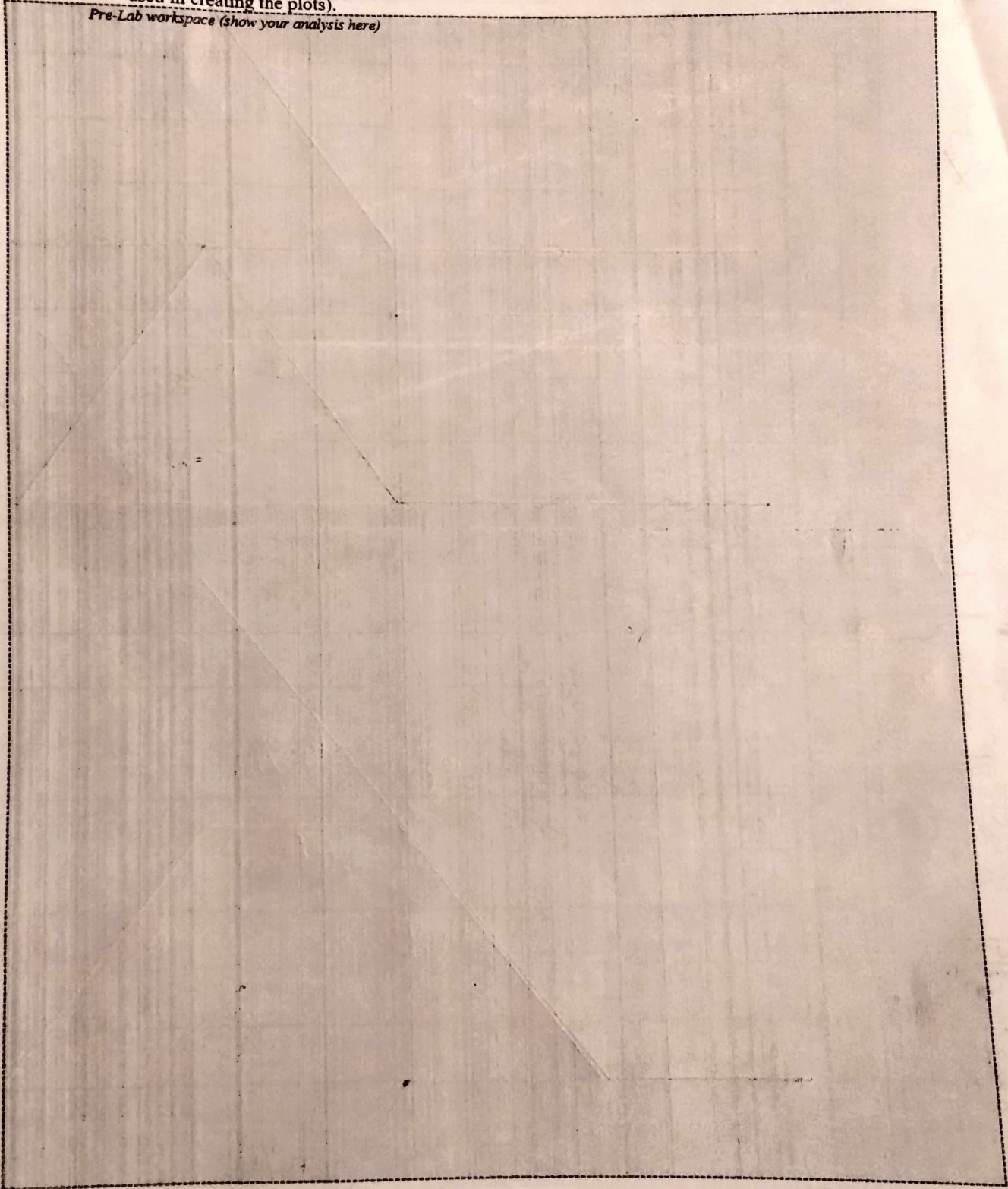

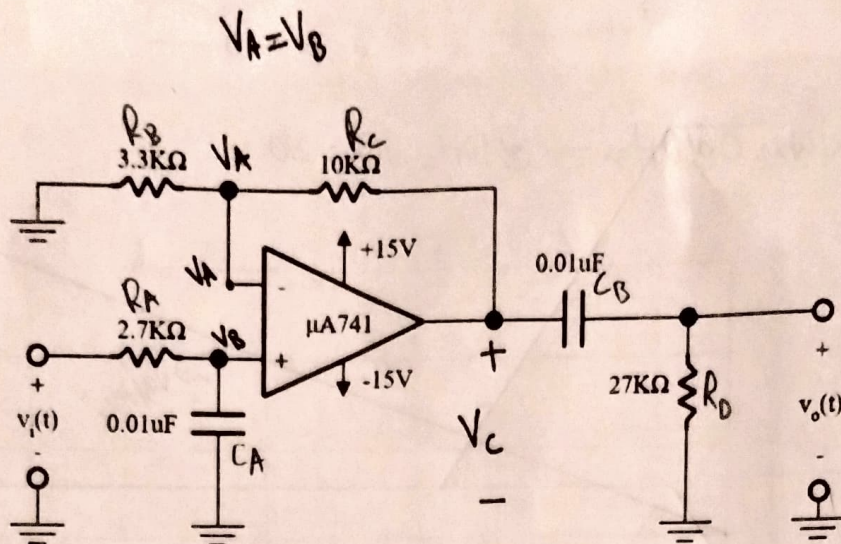


Figure 2.0: A Two Poles-One Zero Circuit

(b) Step 2: Assume that the Op-Amp circuit in Figure 2.0 is working properly.

- i) Derive the transfer function $H(s) = V_o/V_i$.

Pre-Lab workspace (show your analysis here)

~~KCL @ node V_B: $\frac{V_B - V_i}{R_A} + \frac{V_B - V_A}{R_B} = 0$~~

$V_B = \frac{1}{j\omega C_A} V_i \Rightarrow \frac{V_B}{V_i} = \frac{1}{1 + j\omega R_A C_A}$

$V_A = V_B$ KCL @ node V_A: $\frac{V_B - 0}{R_B} + \frac{V_B - V_C}{R_C} = 0 \Rightarrow \frac{V_B}{R_B} = -\frac{V_B + V_C}{R_C}$

$V_0 = \frac{R_D}{R_D + \frac{1}{j\omega C_B}} V_C$ $\frac{V_0}{V_C} = \frac{R_D}{R_D + \frac{1}{j\omega C_B}} = \frac{j\omega R_D C_B}{1 + j\omega R_D C_B} \Rightarrow V_C = \frac{V_B \cdot R_C}{R_B} + V_B = 4.03 V_B$

$\frac{V_0}{V_C} \cdot \frac{V_B}{V_i} \Rightarrow \frac{V_0}{4.03 V_B} \cdot \frac{V_B}{V_i} \Rightarrow \frac{V_0}{4.03 V_i} = \frac{j\omega R_D C_B}{1 + j\omega R_D C_B} \cdot \frac{4.03}{1 + j\omega R_A C_A}$

$\Rightarrow H(s) = \frac{(4.03 \cdot R_D C_B) \cdot j\omega}{(1 + j\frac{\omega}{\frac{1}{R_D C_B}}) \cdot (1 + j\frac{\omega}{\frac{1}{R_A C_A}})} \Rightarrow \frac{0.00109 \cdot j\omega}{(1 + j\frac{\omega}{3703.7}) \cdot (1 + j\frac{\omega}{3703.7})}$

$$① (0.00109)j\omega$$

$$① 20 \log(0.00109) = -59.25$$

$$② j\omega \text{ constant slope } 20 \text{ dB/dec}$$


$$③ \left(1 + \frac{j\omega}{3703.7}\right) \left(1 + \frac{j\omega}{3703.7}\right)$$

$$③ =$$

final

ii)

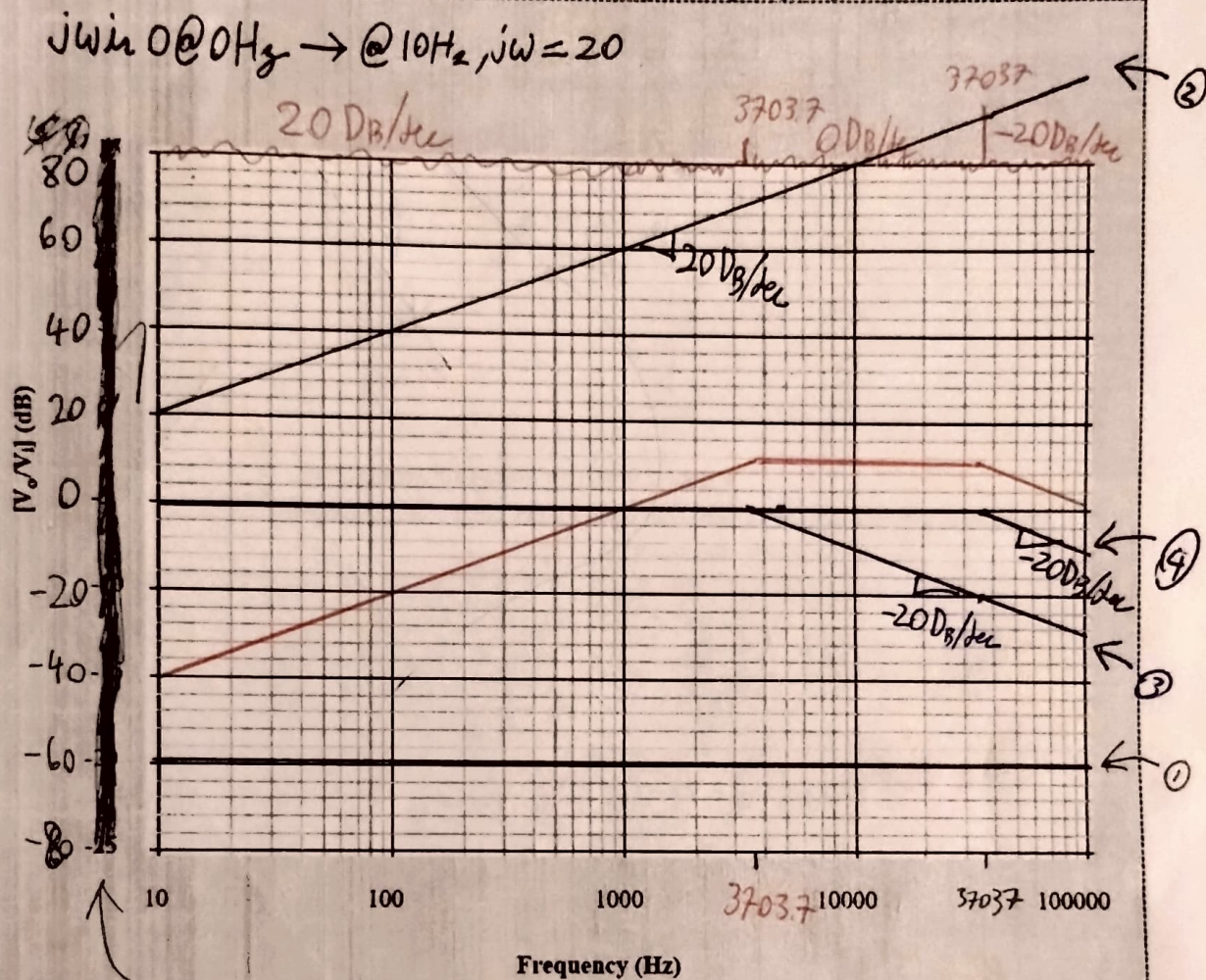Use Graph 2.0 to draw the asymptotic Bode plots for the frequency-response of the circuit:



range not big enough

Graph 2.0 (Gain)

Constant term = 0

① $j\omega = 90^\circ$


② = *final* —

③ =

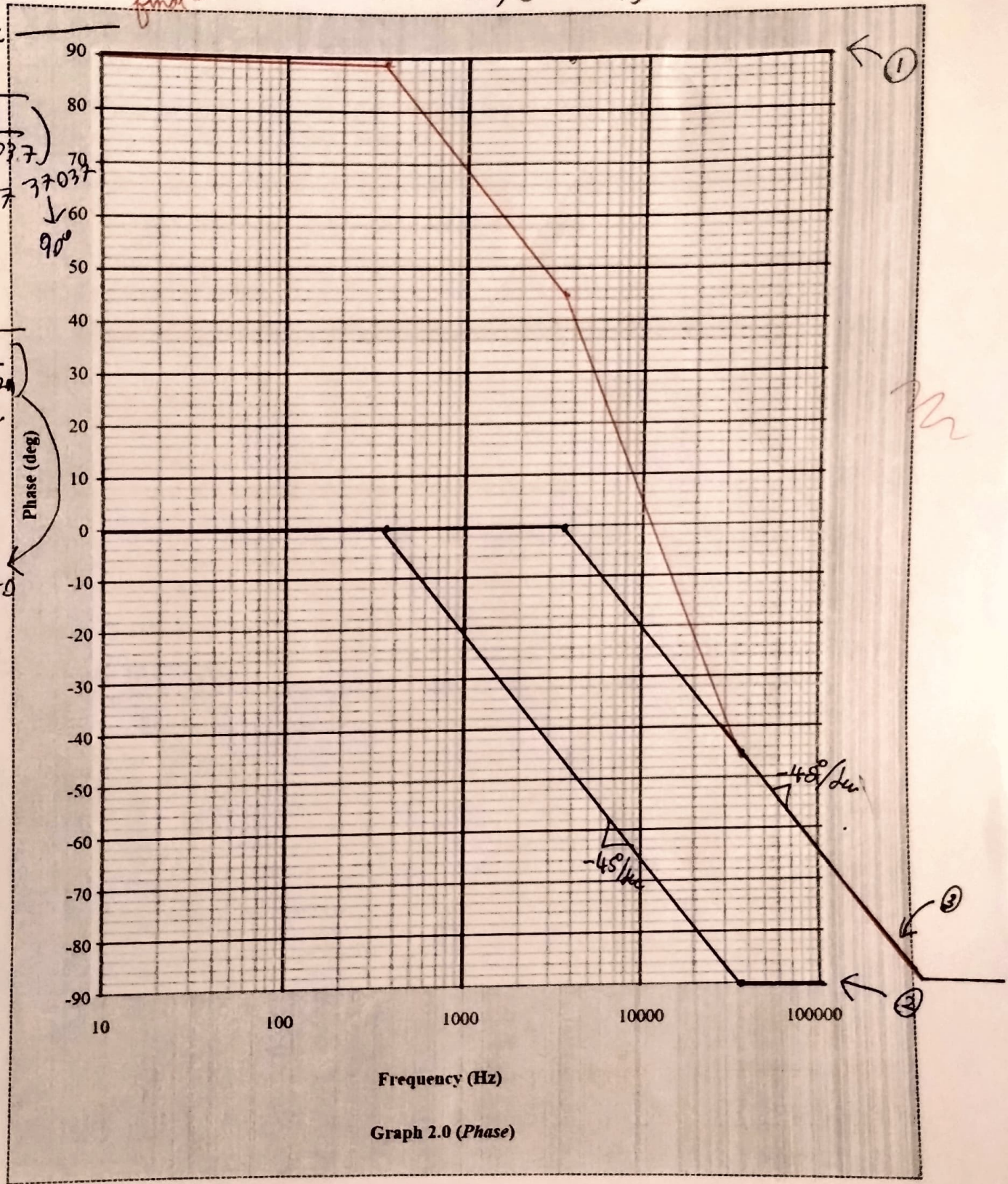(0.00109) · jω ①
 ② $(1 + j\frac{\omega}{3703.7})(1 + j\frac{\omega}{37037})$ ③

$\frac{1}{(1 + j\frac{\omega}{3703.7})}$
 3703.7
 ↓
 0°
 -45°
 90°

$\frac{1}{(1 + j\frac{\omega}{37037})}$
 37037
 ↓
 0°
 -45°
 -90°



- iii) Use Multisim to plot the magnitude in dB and phase in degrees of the frequency-responses of the above circuits, for $10\text{Hz} \leq f \leq 100\text{kHz}$. (Note: Simulate->Instruments->Bode Plotter can be used in creating the plots).

Pre-Lab workspace (show your analysis here)

